

Physics Course - Exercises Summer 2009

Stefan Kremer (kremer@tkm.uni-karlsruhe.de)

Sheet 10

Holger Schmidt (hschmidt@tkm.uni-karlsruhe.de)

30.9.2009

1. Exercise: The tuned circuit

A capacitor with $C = 2 \mu\text{F}$ is put in series to an inductor with $L = 6 \mu\text{H}$ and a resistor with $R = 1 \Omega$.

- (i) Draw the circuit.
- (ii) What kind of functional behaviour will perform the current?
- (iii) Calculate the (possible) period of the oscillation?
- (iv) When will the current I_0 possess its maximum value and how large is it, if initially the current vanishes and the capacitor is charged by $Q_0 = 2 \mu\text{C}$?
- (v) Determine the power $P_R(t)$ which is dissipated in the resistor.

2. Exercise: A capacitor as battery


A charged parallel plate capacitor with area $A = 50 \text{ cm}^2$, distance $d = 1 \mu\text{m}$ and a material with $\epsilon_r = 40$ between the plates is used as voltage source for two parallel connected resistors with resistances $R_1 = 1.5 \text{ k}\Omega$ and $R_2 = 3 \text{ k}\Omega$. Initially the capacitor should deliver a voltage of $U_0 = 3 \text{ V}$.

- (i) Draw the circuit.
- (ii) Which resistance enters in the time dependent part of the current?
- (iii) Calculate the time constant τ .
- (iv) What charge Q_0 has to be placed on the capacitor in order to get the initial voltage?
- (v) State the initial current $I_{2,0}$ through R_2 .
- (vi) What is the charge on the capacitor after $t_4 = 4 \text{ ms}$?
- (vii) How long does the current at R_2 stay larger than $I_c = 0.1 \text{ mA}$?

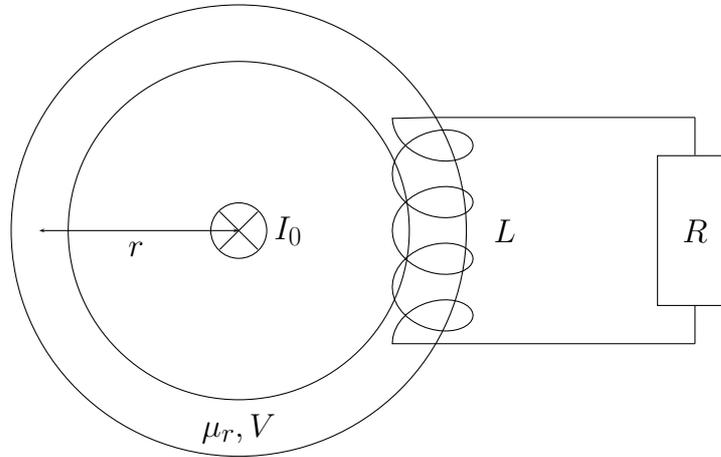3. Exercise: Residual-current device

Background: Residual-current devices are nowadays used in every household. They provide a recoverable and easy to use safety unit for the customers. Such devices consist of a ferromagnetic ring with the power wire on its axis, to enhance its magnetic field. Around the ring a coil is constructed to get a response if the magnetic field collapses or increases rapidly. The resulting current triggers a relay which disconnects the power wire.

We model the relay as a resistor with $R = 15 \Omega$ and the connected coil around the ring should have a self inductance of $L = 5 \text{ mH}$. At $t = 0 \text{ s}$ the former current in the power wire of $I_0 = 1 \text{ A}$ is collapsing instantaneous. Take a relative permeability of $\mu_r = 1000$ for the ferromagnetic ring with radius $r = 10 \text{ cm}$ and volume $V = 100 \text{ cm}^3$ centred around the power wire.



- (i) Determine the magnetic field B_0 at the position of the coil.
- (ii) Calculate the time when the current has decayed to half of its former value \hat{I} .
- (iii) When does it reach the value $\frac{\hat{I}}{e}$?
- (iv) How much energy is dissipated in the resistor depending on the initial current \hat{I} ?
- (v) What is the magnetic energy stored in the coil related to the current and its self inductance?
- (vi) Use the formulas which connect the magnetic field and the self-induction to the geometric quantities of the filled coil to derive a formula stating how the energy stored in the coil is related to the magnetic field inside.
- (vii) Calculate from it the initial current \hat{I} at the relay and the dissipated energy assuming that at $t = 0 \text{ s}$ all the magnetic energy is stored in the ferromagnetic ring.

Note:

- Permittivity of free space: $\epsilon_0 = 8.85 \cdot 10^{-12} \frac{\text{C}}{\text{Vm}}$
- Permeability of vacuum: $\mu_0 = 1.26 \cdot 10^{-6} \frac{\text{Vs}}{\text{Am}}$