

Physics Course - Solutions Summer 2009

Stefan Kremer (kremer@tkm.uni-karlsruhe.de)

Sheet 10

Holger Schmidt (hschmidt@tkm.uni-karlsruhe.de)

30.9.2009


1. Exercise: The tuned circuit

A capacitor with $C = 2 \mu\text{F}$ is put in series to an inductor with $L = 6 \mu\text{H}$ and a resistor with $R = 1 \Omega$.

- (i) Draw the circuit.
- (ii) What kind of functional behaviour will perform the current?
- (iii) Calculate the (possible) period of the oscillation?
- (iv) When will the current I_0 possesses its maximum value and how large is it, if initially the current vanishes and the capacitor is charged by $Q_0 = 2 \mu\text{C}$?
- (v) Determine the power $P_R(t)$ which is dissipated in the resistor.

Solution:

(i)

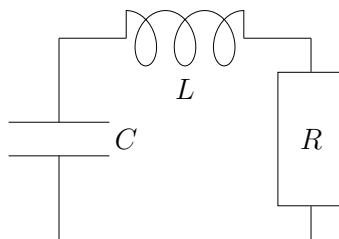

(ii) Since the resistance is small

$$1.0 \Omega = R < \sqrt{\frac{4L}{C}} = 3.5 \Omega$$

the frequency $\Omega = \omega \sqrt{1 - \frac{R^2 C}{4L}}$ with $\omega = \frac{1}{\sqrt{LC}}$ is well defined. Thus the current will perform a damped oscillation.

(iii) The period of that oscillation is given by

$$\underline{\underline{T}} = \frac{2\pi}{\Omega} = \frac{2\pi}{\omega \sqrt{1 - \frac{R^2 C}{4L}}} = \frac{2\pi}{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}} = \underline{\underline{23 \mu\text{s}}}$$

(iv) The maximal value of the current is obtained after one quarter of the period:

$$\underline{t_{1/4}} = \frac{T}{4} = \underline{5.7 \mu\text{s}}$$

Using the trigonometric formula

$$\begin{aligned} \sin(\alpha + \beta) &= \sin \alpha \cos \beta + \cos \alpha \sin \beta \\ \Rightarrow \sin(\arcsin a + \beta) &= a \left(\cos \beta + \sqrt{\frac{1}{a^2} - 1} \sin \beta \right) \end{aligned}$$

the current can be derived by the negative derivation of the solution of the charge:

$$\begin{aligned} I_0(t) &= -\dot{Q} \\ &= -\frac{d}{dt} A e^{-\gamma t} \cos(\Omega t + \phi) \\ &= A \gamma e^{-\gamma t} \cos(\Omega t + \phi) + A \Omega e^{-\gamma t} \sin(\Omega t + \phi) \\ &= A \sqrt{\gamma^2 + \Omega^2} e^{-\gamma t} \frac{\gamma}{\sqrt{\gamma^2 + \Omega^2}} \left(\cos(\Omega t + \phi) + \frac{\Omega}{\gamma} e^{-\gamma t} \sin(\Omega t + \phi) \right) \\ &= A \sqrt{\gamma^2 + \Omega^2} e^{-\gamma t} \sin \left(\Omega t + \phi + \arcsin \frac{\gamma}{\sqrt{\gamma^2 + \Omega^2}} \right) \\ &= A \omega e^{-\gamma t} \sin \left(\Omega t + \phi + \arcsin \frac{\gamma}{\omega} \right) \end{aligned}$$

Since the initial current should vanish the sinus in this last expression have to be zero:

$$I_0(t = 0 \text{ s}) = 0 \quad \Rightarrow \quad \sin \left(\Omega t + \phi + \arcsin \frac{\gamma}{\omega} \right) \quad \Rightarrow \quad \phi = -\arcsin \frac{\gamma}{\omega}$$

Putting this in the solution of the charge the remaining parameter can be obtained by the condition that initial the charge have to be Q_0 :

$$\begin{aligned} Q_0 &= Q(t = 0 \text{ s}) = A \cos \arcsin \frac{\gamma}{\omega} \\ &= A \sqrt{1 - \frac{\gamma^2}{\omega^2}} = A \frac{\sqrt{\omega^2 - \gamma^2}}{\omega} \\ &= A \frac{\Omega}{\omega} \\ \Rightarrow A &= \frac{\omega}{\Omega} Q_0 \end{aligned}$$

Since at the maximum current the sinus function in the formula of the current becomes unity the maximum current will be

$$\underline{I_{\max}} = \frac{\omega^2}{\Omega} Q_0 e^{-\gamma \frac{T}{4}} = \frac{Q_0}{\sqrt{LC - \frac{R^2 C^2}{4}}} e^{-\frac{R}{2L} \frac{T}{4}} = \underline{376 \text{ mA}}$$

(v) Determining the voltage from Ohm's law $R = \frac{U_R(t)}{I(t)}$, the power can be calculated:

$$\underline{P_R(t)} = U_R(t) I(t) = R I(t)^2 = \underline{\underline{\tilde{A} e^{-\tilde{\gamma}} \sin^2(\Omega t)}}$$

$$\text{with } \underline{\tilde{A}} = \frac{R Q_0^2}{LC - \frac{R^2 C^2}{4}} = \underline{141 \text{ mW}}$$

$$\text{and } \underline{\tilde{\gamma}} = \frac{R}{L} = \underline{167 \text{ kHz}} \quad (\underline{\Omega} = 276 \text{ kHz})$$


2. Exercise: A capacitor as battery

A charged parallel plate capacitor with area $A = 50 \text{ cm}^2$, distance $d = 1 \mu\text{m}$ and a material with $\epsilon_r = 40$ between the plates is used as voltage source for two parallel connected resistors with resistances $R_1 = 1.5 \text{ k}\Omega$ and $R_2 = 3 \text{ k}\Omega$. Initially the capacitor should deliver a voltage of $U_0 = 3 \text{ V}$.

- (i) Draw the circuit.
- (ii) Which resistance enters in the time dependent part of the current?
- (iii) Calculate the time constant τ .
- (iv) What charge Q_0 has to be placed on the capacitor in order to get the initial voltage?
- (v) State the initial current $I_{2,0}$ through R_2 .
- (vi) What is the charge on the capacitor after $t_4 = 4 \text{ ms}$?
- (vii) How long does the current at R_2 stay larger than $I_c = 0.1 \text{ mA}$?

Solution:

(i)

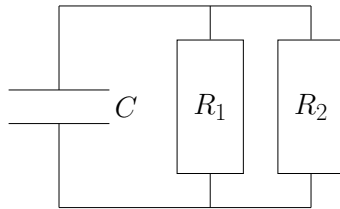

- (ii) The resistance at the capacitor and therefore the one entering the time constant amounts to

$$\underline{R} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \underline{1.0 \text{ k}\Omega}.$$

- (iii) The time constant is determined by

$$\underline{\tau} = RC = R\epsilon_0\epsilon_r \frac{A}{d} = \underline{1.8 \text{ ms}}.$$

- (iv) The charge on the capacitor is given by

$$C = \frac{Q_0}{U_0} \quad \Rightarrow \quad \underline{Q_0} = CU_0 = \epsilon_0\epsilon_r \frac{A}{d} U_0 = \underline{5.3 \mu\text{C}}.$$

- (v) The initial current is given by Ohm's law:

$$R_2 = \frac{U_0}{I_{2,0}} \quad \Rightarrow \quad \underline{I_{2,0}} = \frac{U_0}{R_2} = \underline{1.0 \text{ mA}}$$

(vi) The charge after the time t_4 is given by

$$\underline{\underline{Q(t)}} = Q_0 e^{-\frac{t_4}{\tau}} = \underline{\underline{0.55 \mu\text{C}}}$$

(vii) The current can be derived by the derivation of the charge:

$$I_2(t) = -\dot{Q}_2(t) = I_{2,0} e^{-\frac{t}{\tau}} \quad (\text{with } I_{2,0} = \frac{Q_{2,0}}{\tau} = \frac{Q_{2,0}}{RC})$$


This quantity will be larger than I_c until

$$I_c = I_{2,0} e^{-\frac{t_c}{\tau}} \quad \Rightarrow \quad \underline{\underline{t_c}} = \tau \ln \frac{I_{2,0}}{I_c} = \underline{\underline{4.1 \text{ ms}}}$$

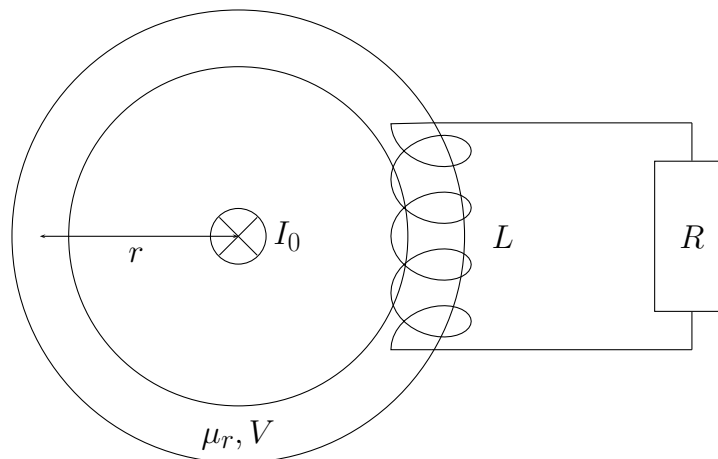3. Exercise: Residual-current device

Background: Residual-current devices are nowadays used in every household. They provide a recoverable and easy to use safety unit for the customers. Such devices consists of a ferromagnetic ring with the power wire on its axis, to enhance its magnetic field. Around the ring a coil is constructed to get a response if the magnetic field collapses or increases rapidly. The resulting current triggers a relay which disconnects the power wire.

We model the relay as a resistor with $R = 15 \Omega$ and the connected coil around the ring should have a self inductance of $L = 5 \text{ mH}$. At $t = 0 \text{ s}$ the former current in the power wire of $I_0 = 1 \text{ A}$ is collapsing instantaneous. Take a relative permeability of $\mu_r = 1000$ for the ferromagnetic ring with radius $r = 10 \text{ cm}$ and volume $V = 100 \text{ cm}^3$ centred around the power wire.



- (i) Determine the magnetic field B_0 at the position of the coil.
- (ii) Calculate the time when the current has decayed to half of its former value \hat{I} .
- (iii) When does it reach the value $\frac{\hat{I}}{e}$?

- (iv) How much energy is dissipated in the resistor depending on the initial current \hat{I} ?
- (v) What is the magnetic energy stored in the coil related to the current and its self inductance?
- (vi) Use the formulas which connect the magnetic field and the self-induction to the geometric quantities of the filled coil to derive a formula stating how the energy stored in the coil is related to the magnetic field inside.
- (vii) Calculate from it the initial current \hat{I} at the relay and the dissipated energy assuming that at $t = 0$ s all the magnetic energy is stored in the ferromagnetic ring.

Solution:

- (i) The magnetic ring is enhanced by the relative permeability to

$$\underline{\underline{B_0}} = \mu_r B_{PW}(r) = \mu_r \mu_0 \frac{I_0}{2\pi r} = \underline{\underline{2.0 \text{ mT}}}$$

- (ii) The half-value period can be evaluated as

$$\frac{\hat{I}}{2} = \hat{I} e^{-\frac{R}{L} t_{1/2}} \Leftrightarrow \underline{\underline{t_{1/2}}} = \frac{L}{R} \ln \frac{\hat{I}}{\hat{I}/2} = \frac{L}{R} \ln 2 = \underline{\underline{0.23 \text{ ms}}}$$

- (iii) The time constant is slight higher than the half-value period and is given by

$$\underline{\underline{\tau}} = \frac{L}{R} \ln e = \frac{L}{R} = \underline{\underline{0.33 \text{ ms}}}$$

- (iv) Due to the time dependent current the voltage will be time dependent, too. Keeping this in mind, the energy can be calculated by integrating the time dependent power:

$$\begin{aligned} \underline{\underline{W_R}} &= \int_0^\infty P(t) dt = \int_0^\infty U_R(t) I(t) dt = \int_0^\infty R I(t)^2 dt = R \hat{I}^2 \int_0^\infty e^{-2\frac{R}{L} t} dt \\ &= R \hat{I}^2 \left(-\frac{L}{2R} \cdot 0 - \left(-\frac{L}{2R} \right) e^0 \right) = \underline{\underline{\frac{1}{2} L \hat{I}^2 = 2.5 \text{ mH} \cdot \hat{I}^2}} \end{aligned}$$

- (v) The energy conservation law states that the energy dissipated in the resistor has to be the one stored in the coil before the decay:

$$\underline{\underline{W_L}} = W_R = \underline{\underline{\frac{1}{2} L \hat{I}^2}}$$

Since the special geometry of the coil is not necessary to derive this result this formula will be valid for every inductive element.

- (vi) From $B = \mu_0 \mu_r \frac{N}{\ell} I$ the current necessary for the magnetic field can be obtained to $I = \frac{B \ell}{\mu_0 \mu_r N}$ which leads to

$$\underline{\underline{W_B}} = W_L = \frac{1}{2} L I^2 = \frac{1}{2} \mu_0 \mu_r \frac{N^2 A}{\ell} \cdot \frac{B^2 \ell^2}{\mu_0^2 \mu_r^2 N^2} = \underline{\underline{\frac{1}{2} \frac{V}{\mu_0 \mu_r} B^2}}$$

(vii) From Lenz law the coil has to generate at $t = 0$ s the magnetic field in the ring. Thus from energy conservation the current can be calculated:

$$W_B = W_L \quad \Rightarrow \quad \frac{1}{2} \frac{V}{\mu_0 \mu_r} B_0^2 = \frac{1}{2} L \hat{I}^2 \quad \Rightarrow \quad \underline{\underline{\hat{I} = \frac{B_0 \sqrt{V}}{\sqrt{\mu_0 \mu_r L}} = 8.0 \text{ mA}}}}$$

With this value the energy dissipated is given by

$$\underline{\underline{W_R = \frac{1}{2} L \hat{I}^2 = 0.16 \mu\text{J}}}}$$

Note:

- Permittivity of free space: $\epsilon_0 = 8.85 \cdot 10^{-12} \frac{\text{C}}{\text{Vm}}$
- Permeability of vacuum: $\mu_0 = 1.26 \cdot 10^{-6} \frac{\text{Vs}}{\text{Am}}$