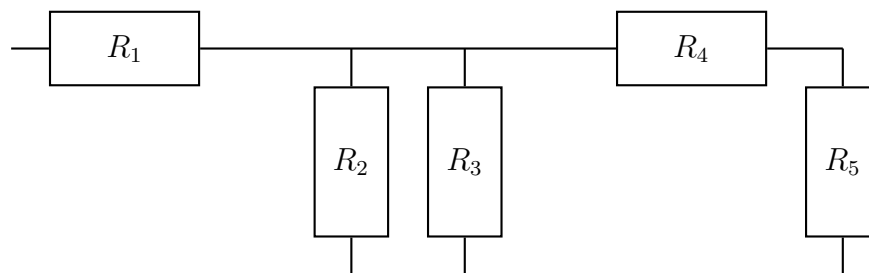


## 1. Exercise:



Consider the above resistor network with resistances of  $R_1 = 2.5 \Omega$ ,  $R_2 = 2 \Omega$ ,  $R_3 = 4 \Omega$ ,  $R_4 = 0.2 \Omega$  and  $R_5 = 0.6 \Omega$ . On it a voltage of  $U_0 = 3.0 \text{ V}$  is applied. The goal is to calculate the power dissipated in the resistor  $R_5$ .

- (a) Redraw the circuit so that parallel and series connections are more apparent (e.g. when all resistors are positioned horizontally).

- (b) Specify therein the substitution resistances  $R_a$  (containing (not only) the resistor  $R_4$ ),  $R_b$  (containing (not only) the resistor  $R_3$ ),  $R_c$  (which do not contain the resistor  $R_1$ ) and  $R_d$  (containing (not only) the resistor  $R_1$ ) which are given either by pure series or parallel connection.

(c) How are the substitution resistances connected to the ones given?

$$R_a =$$

$$R_b =$$

$$R_c =$$

$$R_d =$$

(d) Use Ohm's law to calculate the current  $I_0$  provided by the voltage source.

$$I_0 =$$

(e) Now consider the components of  $R_d$ . What current flows through each of them?

$$I_1 =$$

$$I =$$

(f) Use again Ohm's law to determine the voltage drop on its components.

$$U_1 =$$

$$U =$$

(g) Next focus on the components of  $R_c$ . What voltage drop on each of its components?

$$U =$$

$$U =$$

(h) Find the current through each of its components.

$$I =$$

$$I =$$

(i) Finally consider the components of  $R_a$  and state the current which flows through them.

$$I_4 =$$

$$I =$$

(j) Calculate the voltage drop along its components.

$$U_4 =$$

$$U =$$

(k) Use your results to give the power dissipated in the resistor  $R_5$ .

$$\underline{\underline{P_5}} =$$