

**1. Exercise:**

A coil with self inductance  $\mathcal{L} = 5.0 \text{ H}$  is placed across the terminals of a battery labeled  $U = 12 \text{ V}$  with inner resistance  $R = 15 \Omega$ .

- What is the final current  $I_f$ ?
- State the time constant  $\tau$ .
- When has the current reached 75% of its maximum value?
- How large would be the maximum current  $\hat{I}$  if the battery was replaced by an AC-source with frequency  $\omega = 50 \text{ s}^{-1}$  and maximum strength  $\hat{U} = U$ ?

**Solution:**

- At the final situation the coil does not contribute. Therefore the current is given by Ohm's law:

$$\underline{I_f} = \frac{U}{R} = \underline{0.8 \text{ A}}$$

- The time constant of this  $R\mathcal{L}$ -circuit is given by

$$\underline{\tau} = \frac{\mathcal{L}}{R} = \underline{0.33 \text{ s}}.$$

- After the battery is connected to the coil, the current will increase exponentially:

$$0.75I_f = I_f (1 - e^{-t/\tau}) \quad \Rightarrow \quad \underline{t} = \tau \ln(4) = \underline{463 \text{ ms}}$$

- The maximum current can be determined by the inductive reactance (since the inner resistance of the battery is replaced as well):

$$\underline{\hat{I}} = \frac{\hat{U}}{X_L} = \frac{\hat{U}}{\omega \mathcal{L}} = \underline{48 \text{ mA}}$$

## 2. Exercise:

A capacitor with  $C = 4.0 \mu\text{F}$  is charged to  $U = 24 \text{ V}$  and then connected across two serially connected resistors with  $R = 100 \Omega$ .

- Find the initial charge  $Q_0$  on the capacitor.
- Determine the initial current  $I_0$  through the resistor.
- What is the time constant  $\tau$ ?
- How much charge  $Q$  is on the capacitor after  $t = 4 \mu\text{s}$ ?
- Sketch the time dependence of the current  $I_1(t)$  through one of the resistors and mark where  $I_0$  and  $\tau$  can be found in the diagram.

## Solution:

- The initial charge is determined by the definition of the capacitance:

$$\underline{\underline{Q_0}} = CU = \underline{\underline{96 \mu\text{C}}}$$

- The initial current is given by Ohm's law:

$$\underline{\underline{I_0}} = \frac{U}{2R} = \underline{\underline{0.12 \text{ A}}}$$

- The time constant for a  $RC$ -circuit where the total resistance is  $2R$  was found to be


$$\underline{\underline{\tau}} = 2RC = \underline{\underline{0.8 \text{ ms}}} .$$

- The charge is exponentially decreasing:

$$\underline{\underline{Q(t)}} = Q_0 e^{-t/\tau} = \underline{\underline{95.5 \mu\text{C}}}$$

- The current is given by the time derivative of the charge:
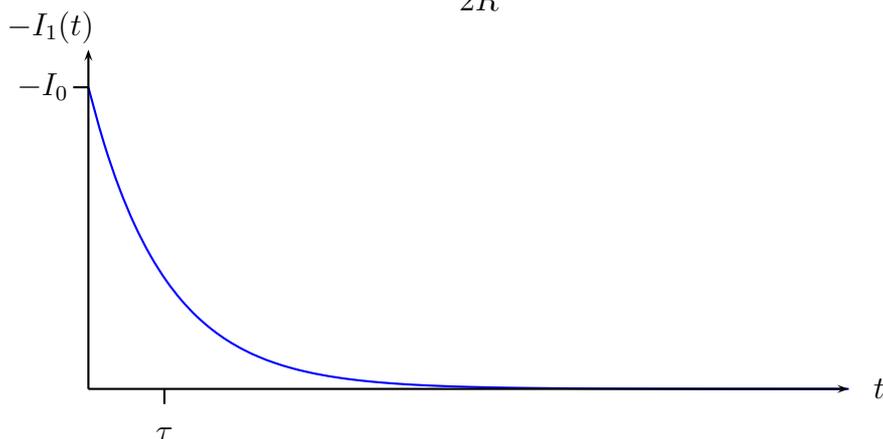
$$I_1(t) = -\frac{U}{2R} e^{-t/(2RC)} = -I_0 e^{-t/\tau}$$



- Note that in this exercise both times the total resistance  $2R$  is present in the denominator as well as in the exponent in the current. However, in a parallel connection the current would divide into two currents flowing through the resistors and therefore different values would be present in general.

### 3. Exercise:

A capacitor with  $C = 2.0 \mu\text{F}$  is charged to  $U = 20 \text{V}$  and is then connected across an inductor with  $\mathcal{L} = 6.0 \mu\text{H}$ .

- What is the frequency  $f$  of the oscillation?
- Find the maximum value of the charge on the capacitor  $Q_0$ .
- Determine the maximum value of the current  $I_0$ .

### Solution:

- For this situation Kirchhoff's voltage law reads

$$0 = \frac{Q}{C} + \mathcal{L}\ddot{Q} \quad \Rightarrow \quad \ddot{Q} = -\frac{1}{\mathcal{L}C}Q$$

which is the differential equation of the harmonic oscillator. Therefore the solution is given by

$$Q(t) = Q_0 \cos(\omega t) \quad \text{with} \quad \omega = \frac{1}{\sqrt{\mathcal{L}C}}$$

where the initial charge  $Q_0$  which is initially at the capacitor was used. Hence, the frequency is given by

$$\underline{\underline{f}} = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{\mathcal{L}C}} = \underline{\underline{4.6 \cdot 10^4 \text{ Hz}}} .$$

- The maximum charge which is the initial charge is determined by the definition of the capacitance:

$$\underline{\underline{Q_0}} = CU = \underline{\underline{40 \mu\text{C}}}$$

- The maximum current is determined by the maximum of the derivative of the charge:

$$\underline{\underline{I_0}} = \max_t(\dot{Q}) = \max_t(-Q_0\omega \sin(\omega t)) = \omega Q_0 = \omega CU = \underline{\underline{11.5 \text{ A}}}$$

This is like the current of the coil as an AC-source using the capacitive reactance,  $I_0 = \frac{U}{X_C}$ , only that the frequency of the AC-source depend as well on the capacitance. It can as well be viewed as the capacitor as an AC-source in an inductive circuit. The current is therefore given by the inductive reactance  $I_0 = \frac{U}{X_L}$  where the frequency of the source depend as well on the given inductance.