

1. Exercise:

A Nichrome wire ($\rho_s = 1.0 \cdot 10^{-6} \Omega\text{m}$) has a radius of $r = 6.5 \text{ mm}$.

- What length ℓ of a wire is needed to obtain a resistance of $R = 20 \text{ m}\Omega$?
- Find the magnitude of the electric field \mathcal{E} in the wire if it is carrying a current of $I = 1.3 \text{ A}$.
- What would be the capacitance C of a similar isolating wire made of Barium titanate with $\epsilon_r = 4000$ (and metallic bases)?
- How many charges Q would be on its bases if the same electric field is present?

Solution:

- (a) From the definition of the specific resistance it is found:

$$R = \rho_s \frac{\ell}{\pi r^2} \quad \Rightarrow \quad \underline{\underline{\ell}} = \frac{R\pi r^2}{\rho_s} = \underline{\underline{2.7 \text{ m}}}$$

- (b) The electric field is given by

$$\underline{\underline{\mathcal{E}}} = \frac{U}{\ell} = \frac{IR}{\ell} = \frac{I\rho_s}{\pi r^2} = \underline{\underline{9.8 \frac{\text{mV}}{\text{m}}}}$$

- (c) The capacitance is determined to

$$\underline{\underline{C}} = \epsilon_0 \epsilon_r \frac{\pi r^2}{\ell} = 1.8 \cdot 10^{-12} \text{ F} = \underline{\underline{1.8 \text{ pF}}}$$


- (d) By the definition of the capacitance a charge of

$$C = \frac{Q}{U}, \quad U = \mathcal{E}\ell \quad \Rightarrow \quad \underline{\underline{Q}} = \mathcal{E}\ell C = \underline{\underline{4.6 \cdot 10^{-14} \text{ C}}}$$

is needed.

2. Exercise:

Consider the following resistor network:

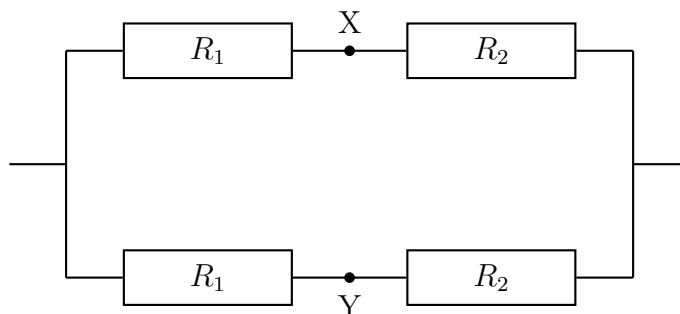

The resistors have the resistances $R_1 = 3.0\ \Omega$ and $R_2 = 2.0\ \Omega$.

- Determine the equivalent resistance R_{tot} .
- What would be the current I_0 through the whole circuit if a voltage of $U_0 = 1.5\ \text{V}$ is applied?
- How large is the current I_1 which flows through a resistor with resistance R_1 in this case?
- Find the voltages U_1 and U_2 which drop at the resistors with resistance R_1 and R_2 .
- What powers P_1 and P_2 are dissipated at the resistors R_1 and R_2 ?
- Determine the electrical potential at the points X and Y if the left end of the circuit lies at the potential of $\phi_0 = 2.0\ \text{V}$ while the right end is at a lower value.
- Which voltage U_{XY} drops between the points X and Y and how large is the current I_{XY} which flows in a wire connecting these points?

Solution:

- (a) The total / equivalent resistance is given by

$$\underline{\underline{R_{\text{tot}}}} = \frac{1}{\frac{1}{R_1+R_2} + \frac{1}{R_1+R_2}} = \frac{R_1 + R_2}{2} = \underline{\underline{2.5\ \Omega}}.$$

- (b) The current can be determined by Ohm's law:

$$R_{\text{tot}} = \frac{U_0}{I_0} \quad \Rightarrow \quad \underline{\underline{I_0}} = \frac{U_0}{R_{\text{tot}}} = \underline{\underline{0.60\ \text{A}}}$$

- (c) Since the voltage does not change if three wires connect each other and the current which flows through R_1 is the same as the one which flows through R_2 the current through R_1 is found to be

$$R_1 + R_2 = \frac{U_0}{I_1} \quad \Rightarrow \quad \underline{\underline{I_1}} = \frac{U_0}{R_1 + R_2} = \underline{\underline{0.30\ \text{A}}}.$$

- (d) The voltages can be calculated by Ohm's law. They can be checked by Kirchhoff's voltage law:

$$\begin{aligned}
 R_1 &= \frac{U_1}{I_1} & \Rightarrow & \quad \underline{U_1} = R_1 I_1 = \underline{0.90 \text{ V}} \\
 R_2 &= \frac{U_2}{I_1} & \Rightarrow & \quad \underline{U_2} = R_2 I_1 = \underline{0.60 \text{ V}} \\
 U_1 + U_2 &\stackrel{!}{=} U_0 & \checkmark &
 \end{aligned}$$

- (e) By the definition of the electric power the values can be found. They can be checked by the conservation of energy:

$$\begin{aligned}
 \underline{P_1} &= U_1 I_1 = \underline{0.27 \text{ W}} \\
 \underline{P_2} &= U_2 I_1 = \underline{0.18 \text{ W}} \\
 2(P_1 + P_2) &\stackrel{!}{=} U_0 I_0 = 0.90 \text{ W} & \checkmark
 \end{aligned}$$

- (f) Since the voltage is the difference in the electrical potential which drops at R_1 the result is given by

$$\underline{\phi_X = \phi_Y} = \phi_0 - U_1 = \underline{1.1 \text{ V}} .$$

It can be checked if the potential in the rest of the circuit is determined:

$$\phi_X - U_2 = 0.5 \text{ V} \stackrel{!}{=} \phi_0 - U_0 \quad \checkmark$$

- (g) Since both points are lying on the same electrical potential there can not be a voltage drop. However, if there is no voltage drop no current will flow:

$$\underline{U_{XY} = 0} \quad \underline{I_{XY} = 0}$$

Note:

The Vacuum permittivity is given by $\epsilon_0 = 8.85 \cdot 10^{-12} \frac{\text{As}}{\text{Vm}}$