

## Pre-Semester 2010 - Physics Course - Extra Tutorial

STÉPHANE NGO DINH  
STEPHANE.NGODINH@KIT.EDU

Solution 13  
23.09.2010

## 1. RC-Circuit

Consider a capacitor  $C$  which is connected in series to two parallel connected resistors  $R_1$  and  $R_2$ . Initially, the charge  $Q$  on (one of) the capacitor's plate, is  $Q(t = 0) = Q_0$ .

- Find the charge  $Q(t)$  in the capacitor as a function of time  $t$  if initially it is  $Q(t = 0) = Q_0$ . What is the time constant  $\tau$ ?
- What is the initial (total) current  $I_0$  through the resistors? What is the initial voltage  $U_0$  across the capacitor?
- If after time  $t_{1/2} = 20.79$  ms the charge  $Q$  has dropped to 50% of its initial value, what is  $\tau$ ?
- In the situation of (1c): What is  $R_1$  if  $R_2 = R_1$ ,  $Q_0 = 0.3$  C and  $U_0 = 200$  V?

**Solution:**

- The total resistance of the parallel connection of the two resistors is

$$R = \frac{1}{1/R_1 + 1/R_2}.$$

Kirchhoff's rule gives the "equation of motion"

$$0 = Q/C + IR = Q/C + \dot{Q}R.$$

With the initial condition  $Q(t = 0) = Q_0$  the solution is

$$Q(t) = Q_0 e^{-t/\tau}$$

where the time constant is

$$\tau = RC = \frac{C}{1/R_1 + 1/R_2}.$$

- The initial current is

$$I_0 = \dot{Q}(t = 0) = -\frac{Q_0}{RC}.$$

The initial voltage is

$$U_0 = Q_0/C.$$

Thus (up to signs) Ohm's law is satisfied:

$$|I_0| = |U_0|/R.$$

(c)  $t_{1/2}$  is defined by the equation

$$Q(t_{1/2}) = \frac{1}{2}Q_0 \Leftrightarrow e^{-t_{1/2}/\tau} = \frac{1}{2} \Leftrightarrow -t_{1/2}/\tau = \ln \frac{1}{2} = -\ln 2$$

(d) 
$$\Leftrightarrow \tau = \frac{t_{1/2}}{\ln 2} = 30.0 \text{ ms.}$$

$$\begin{aligned} U_0 = Q_0/C &\Rightarrow C = Q_0/U_0, \\ \tau = RC &\Rightarrow R = \tau/C = \tau U_0/Q_0, \\ R = R_1/2 &\Rightarrow R_1 = 2R = 2\tau U_0/Q_0 = 40 \Omega. \end{aligned}$$

## 2. LR-Circuit

Consider a coil with inductance  $L$  and a resistor  $R$  connected in series. Assume that for  $t < 0$  they were additionally connected in series to a voltage source with voltage  $U_0$  driving a stationary current  $I_0$ . At  $t = 0$  the voltage source is removed.

- What is  $I_0$  (in terms  $L$ ,  $R$ , and  $U_0$ )?
- Find the current  $I(t)$  through the resistor as a function of time  $t$ . What is the time constant  $\tau$ ?
- What is the voltage drop  $U_R(t)$  across the resistor at time  $t$ ?
- Sketch  $U_R(t)$  and mark  $U_0$  and  $\tau$  in the diagram.

**Solution:**


- Ohm's law:  $I_0 = U_0/R$ .
- Kirchhoff's rule:  $= IR + L\dot{I}$ .  
Solution with initial condition  $I(t = 0) = I_0$  is  $I(t) = I_0 e^{t/\tau}$  with time constant

$$\tau = L/R.$$

- Again Ohm's law:

$$U_R(t) = RI(t) = RI_0 e^{-t/\tau} = U_0 e^{-t/\tau}.$$

- Plot:

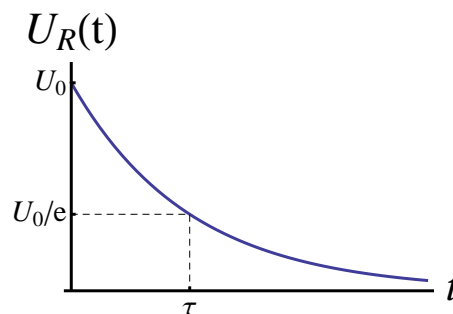

## 3. LC-Circuit

A parallel-plate capacitor with capacitance  $C$ , which has been charged by a voltage  $U_0$ , is connected at  $t = 0$  to an ideal coil with inductance  $L$ . No voltage sources are present (hence, the initial current is  $I(t = 0) = 0$ ).

- (a) What is the maximal charge  $Q_0$  in the capacitor?  
 (b) Give the charge  $Q(t)$  in the capacitor as a function of time  $t$ .  
 (c) What is the maximal current  $I_0$  and at what time  $t_0$  is it reached,  $|I(t_0)| = I_0$ , the first time?  
 (d) Sketch  $Q(t)$  as well as the current  $I(t) = \dot{Q}(t)$  and mark  $Q_0$ ,  $I_0$ ,  $t_0$  and the period  $T$  in the diagrams.  
 (e) Assume that, in case the capacitor is empty, current oscillates with frequency  $f_0 = T^{-1} = 80$  kHz. What would be the frequency  $f_r$  in case the capacitor is filled with a dielectric material with relative permittivity  $\epsilon_r = 16$ ?  
 (f) Assume now that a resistor is connected in series to  $L$  and  $C$ . Give a *qualitative* sketch of  $I(t)$  for this case. (Do not calculate anything!)

**Solution:**

- (a) Initially, the capacitor is maximally charged:  $Q_0 = CU_0$ .  
 (b) Kirchhoff's rule gives

$$0 = Q/C + L\dot{I} = Q/C + L\ddot{Q} \Leftrightarrow \ddot{Q} + \frac{1}{LC}Q = 0.$$

Differential equation well known, describes harmonic oscillation. Initial conditions read

$$Q(t=0) = Q_0, \quad \dot{Q}(t=0) = 0.$$


The solution is

$$Q(t) = Q_0 \cos(\omega t) \text{ with } \omega = \frac{1}{\sqrt{LC}}.$$

- (c) The current is  $I(t) = \dot{Q}(t) = -Q_0\omega \sin(\omega t)$ . It is maximal the first time, when  $\sin(\omega t) = 1$  the first time, that means for

$$\omega t_0 = \frac{\pi}{2} \Leftrightarrow t_0 = \frac{\pi}{2\omega}.$$

- (d) Plots:

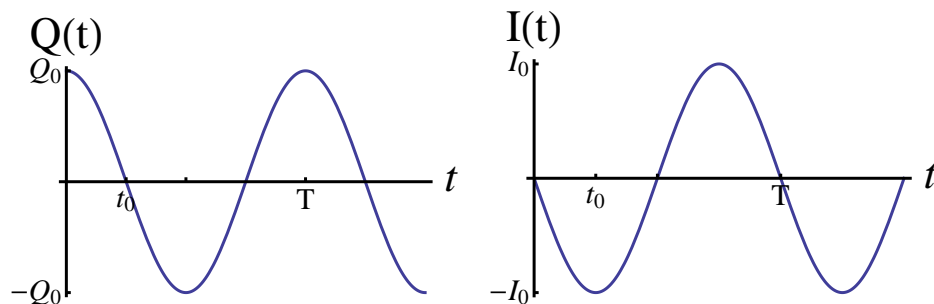

- (e) For an empty capacitor the frequency is

$$80 \text{ kHz} = f_0 = \frac{1}{2\pi} \frac{1}{\sqrt{LC_0}}.$$

For a filled capacitor it is

$$f_r = \frac{1}{2\pi} \frac{1}{\sqrt{LC_r}} = \frac{1}{2\pi} \frac{1}{\sqrt{L\epsilon_r C_0}} = \frac{f_0}{\sqrt{\epsilon_r}} = 20 \text{ kHz}.$$

(f) Plot:

